

# Circuit Theory and Electronics Fundamentals

Department of Electrical and Computer Engineering, Técnico, University of Lisbon

## T3's Laboratory Report

### Group 5

Carlos Ribeiro (96364), João Diniz (96416), Paulo Clemente (96462)

May 5, 2021

## Contents

<b>1</b>	<b>Introduction</b>	<b>1</b>
<b>2</b>	<b>Simulation analysis</b>	<b>2</b>
2.1	Simulating the AC/DC converter for 10 periods . . . . .	2
2.2	Output voltage level . . . . .	3
2.3	Output of the Envelope Detector and voltage Regulator circuits . . . . .	4
2.4	Output voltage ripple . . . . .	7
2.5	$v_0 - 12$ plot . . . . .	7
<b>3</b>	<b>Theoretical Analysis</b>	<b>8</b>
3.1	Envelope detector and voltage regulator plot . . . . .	8
<b>4</b>	<b>Conclusion</b>	<b>9</b>

## 1 Introduction

The objective of this laboratory assignment is to choose the architecture of the envelope and voltage regulator circuits in order to have the best merit (M) possible.

Firstly, we started this laboratory writing an NGspice script that simulates the AC/DC converter and measure the output voltage level and voltage ripple , plotting the the voltages at the output of the envelope detector and voltage regulator circuits and the output AC component + DC deviation).

Then, using octave, we have created a theoretical model able to predict the output of the envelope detector and voltage regulator circuits, plotting the same results as in simulation anal-

ysis (using theoretical analysis). Finally, also the output DC level and the voltage ripple were computed.

The merit is calculated using the following expression:

$$M = \frac{1}{\text{Cost}(\text{ripple}(v_0) + \text{average}(v_0 - 12) + 10^{-6})} \quad (1)$$

Where:

Cost = cost of resistors + cost of capacitors + cost of diodes

Cost of Resistors = 1 monetary unit per kOhm

Cost of capacitor = 1 monetary unit per  $\mu$  F

Cost of diodes = 0.1 Monetary units per diode

Firstly, we have created a simple circuit and then we were updating the circuit to improve the figure of merit. The final circuit obtained is the one shown below in figure (Fig.1):

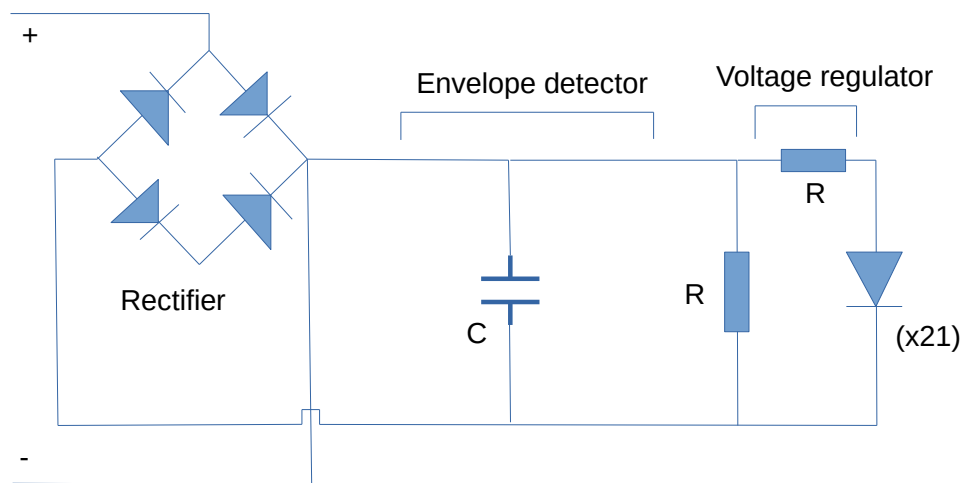


Figure 1: Final circuit

The individual costs of the components used:

- Diodes - cost: 2.3MU;
- Capacitor - 5MU;
- Resistances - 55MU.

The data used was the following:

Name	Value
$R_1$	65 k $\Omega$
$R_2$	7.26 k $\Omega$
$C$	20 $\mu$ S
Diodes	19 Units

## 2 Simulation analysis

### 2.1 Simulating the AC/DC converter for 10 periods

As said in the introduction, the first step to this laboratory assignment was to simulate a simple AC/DC converter in NGSpice, the circuit features an ideal transformer, using a current

controlled voltage source as well as a voltage controlled current source as explained by the professor in a previous lecture, as well as an envelope detector and a voltage regulator.

This AC/DC converter was simulated for 10 periods and all the analysis were made measuring on a  $5e-5$  step in order to evaluate at least 1000 points during the 10 periods. In order to calculate this step we used the frequency of the AC source to know the period and then we multiplied this period by 10 in order to get the total time. We then divided the total time by 1000 points and made the step even smaller than that in order to make sure it had more than 1000 points but not too small that the program ran slowly.

This circuit was first made simple and was elaborated along the way, making it output the correct voltage, increasing the merit figure.

## 2.2 Output voltage level

After describing the circuit we made NGSpice measure the average output voltage and using a transient analysis we plotted both the average and the signal of the output voltage in the same graph.

The table and the graph below show the results we got.

Name	Value [V]
mean(v(n5)-v(n3))	1.200025e+01

 


Figure 2: Plot of the average and the signal of the Output Voltage.

## 2.3 Output of the Envelope Detector and voltage Regulator circuits

The output voltages of both the Envelope Detector as well as the Voltage Regulator circuits were plotted and put each in a different graph as well as a graph with both voltages plotted.

The three graphs are in the images below.

 


Figure 3: Envelope Detector Output Voltage.

 


Figure 4: Voltage Regulator Output Voltage.

 


Figure 5: Envelope Detector and Voltage Regulator Output Voltages.

## 2.4 Output voltage ripple

We then made NGSpice measure the output voltage ripple, that is the difference between the maximum and the minimum values of the signal.

The result we got is in the table below.

Name	Value [V]
maximum(v(n5)-v(n3))-minimum(v(n5)-v(n3))	5.616238e-03

## 2.5 $v_0 - 12$ plot

Lastly, we plotted  $v_0 - 12$ , which corresponds to the output AC component plus the DC deviation.

The plot can be seen in the image below.

 


Figure 6: Output AC component + DC deviation.

### 3 Theoretical Analysis

In this section are shown the obtained results using a suitable theoretical model able to predict the output of the Envelope Detector and voltage Regulator circuits.

#### 3.1 Envelope detector and voltage regulator plot

In this plot we can see the output voltage of the envelope and voltage regulator circuits. The envelope detector restricts the voltage's amplitude and the voltage regulator decreases the ripple.



## 4 Conclusion

Summing up, this laboratory provided us the opportunity to understand how the envelope detector and voltage regulator circuits work and, also, how to improve their efficiency.

Finally, we are going to compare the results from simulation and theoretical analysis side by side:

Name	Value
Resistor Cost	7.226000e+01
Capacitor Cost	2.000000e+01
Diode Cost	2.300000e+00
Total Cost	9.456000e+01
Merit	2.636305e-01

 


Figure 7: Theoretical Output Voltage Level

 


Figure 8: Simulation Output Voltage Level

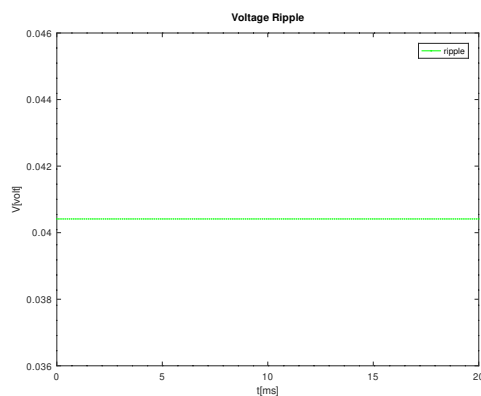


Figure 9: Theoretical Ripple

Ripple	Value [V]
maximum(v(n5)-v(n3))-minimum(v(n5)-v(n3))	5.616238e-03

Figure 10: Simulation Ripple

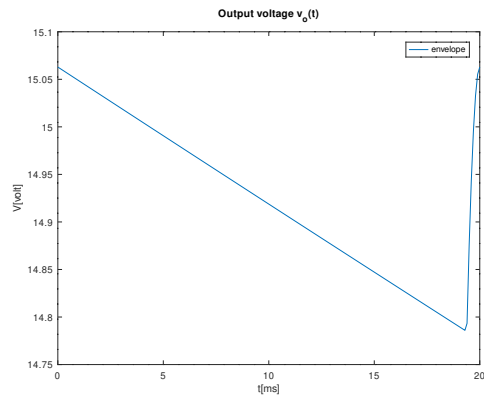


Figure 11: Theoretical Envelope Detector Voltage Level

 


Figure 12: Simulation Envelope Detector Voltage Level

 


Figure 13: Theoretical Voltage Regulator Voltage Level

 


Figure 14: Simulation Voltage Regulator Voltage Level

 


Figure 15: Theoretical  $v_0 - 12$  Voltage Level

 


Figure 16: Simulation  $v_0 - 12$  Voltage Level